NCL Low Power Design Example Problems

1) Draw the schematic of a static TH24 gate and its MTCMOS version.

2) Consider utilizing MTCMOS NCL threshold gates to build a large circuit. Compared to its non-MTCMOS original version, where could the area difference (both overhead and reduction) come from?